

Engineering Sciences 31/Computer Science 56

Final Project

Liane Makatura and Stylianos Tegas

August 31, 2015

Abstract

The advent of digital electronics has ushered in an era of rapid innovation and discovery. These electronics have infiltrated nearly every aspect of our daily lives, holding significant influence over activities from education to personal communication. We decided to explore the influence of digital electronics in the entertainment industry, pursuing the creation of a polyphonic keyboard. The notes of this keyboard span one full octave, from C4 (middle C) to C5, including all sharps and flats. It also implements a sustain pedal, which allows the user to suspend notes even after the corresponding key has been released.

Contents

| | |
|--|-----------|
| Contents | 2 |
| 1 Introduction | 3 |
| 2 Design Solution | 3 |
| 2.1 Specifications | 3 |
| 2.2 Operating Instructions | 4 |
| 2.3 Theory of Operation | 5 |
| 2.4 Construction and Debugging | 8 |
| 3 Justification and Evaluation | 9 |
| 4 Conclusions | 10 |
| 5 Acknowledgements | 11 |
| 6 References | 11 |
| 7 Appendices | 12 |
| 7.1 System Level Diagrams | 12 |
| 7.2 Programmed Logic | 14 |
| 7.3 Memory Map | 44 |
| 7.4 Waveform Graphs | 45 |
| 7.5 Data Sheets | 46 |
| 7.6 Computer Programs | 46 |

1 Introduction

While digital electronics have a wide range of usefulness in various applications, generating sound is rather difficult without a specific hardware setup in place. Further complicating things, generating more than one note at a time (polyphony) is practically impossible without multiple FPGA systems. Thus, the problem to solve is twofold: how can one generate sound, and how can one generate superpositions of sounds?

2 Design Solution

2.1 Specifications

Inputs:

1. Note Buttons ($C4 - C5$)
2. Sustain Switch

The circuit receives a series of button presses based on the above possible inputs, as well as a possible switch signal. Based on the buttons pressed, the circuit creates addresses for a wave generator lookup table that increment in certain step sizes. These addresses are used to find the corresponding value of the wave for each note. These values are added together on the other side of the lookup table and then normalized. This final value is then sent through a digital to analog converter before being played on a speaker. If the sustain switch is closed, then even after a button is released, the circuit continues to play that note.

2.2 Operating Instructions

Assembly:

Materials:

1. FPGA (Nexys 3) with its microUSB cable
2. Computer (must have Xilinx and Adept software)
3. Required VHDL files
4. Pmod DA2 - Digital to Analog Converter
5. Pmod AMP2 - Sound Amplifier
6. Pmod BTN - Four Push Buttons (x4)
7. Pmod Cable Kit, 6 pin (x5)

Assembly of the keyboard is fairly straightforward. First, gather the above materials. Assemble the cable kits and place one in each of the top halves of the 12 pin connectors on the FPGA (JA, JB, JC, JD). Take the final cable kit and place it in the bottom half of the JD 12 pin connector. Attach the four Pmod BTNs to the cable kits placed in the top halves of the 12 pin connectors. Attach the Pmod DA2 to the cable kit in the bottom half of the JD 12 pin connector, then attach the Pmod AMP2 to the output of the Pmod DA2. The Pmod AMP2 is modified such that its 4th pin (the shutdown pin) is tied to V_{cc} so that it is always ready to receive data.

Connect the FPGA board to the computer. Assemble the required files in the ISE Design Kit software, then generate a programming file. Finally, open the Adept software, and program the FPGA. Congratulations, you have a functional polyphonic keyboard!

Usage

To use our keyboard, just push any combinations of the buttons on the Pmod BTNs! The top left button on the Pmod connected to the JC 12 pin connector does not connect to an input into the circuit, a feature shared by the top buttons on the Pmod connected to the JA 12 pin connector. To sustain notes, simply flip the switch located at T10 on the FPGA.

2.3 Theory of Operation

Each section in the block diagram of the circuit is explained in more detail below. The operation of the circuit is as follows:

Slow Clock

This is a clock divider that runs the majority of the circuit. It is a clock that runs six times slower than the master clock (100MHz). This slow clock is required for the circuit because of the inherent latency in the wave generator lookup table. Since it takes 6 clock cycles for the lookup table to generate an output after it has received an input, the rest of the circuit must run 6 times slower than the lookup table to compensate and not generate unwanted outputs.

The slow clock takes in the master clock as input. It counts to three, and when it reaches three, it flips the value of its internal signal. The internal signal is outputted constantly. Thus, the block acts as a clock running at $(100 / 6) = 16.67\text{MHz}$.

Sampler Counter

This is a counter that creates the note sampling rate of 44.1kHz, used almost ubiquitously in audio digital recording. This counter is required for the circuit because it reduces the number of samples taken, which in turn allows us to create sounds that humans will be able to hear. This is because of the way that direct digital synthesis evaluates and creates tones (i.e. the output frequency is directly proportional to the sampling frequency).

The sampler counter takes the slow clock as input. It counts to 378 before outputting an enable signal. This enable signal is eventually fed into both the note address lookup/update array and the select counter.

Note Address

This is a set of two arrays, used to index the correct sine value to generate its corresponding note. This set of arrays is required for the circuit in order to generate the correct tones from the wave generator lookup table.

The arrays receive input from the select counter. When the enable is asserted, each of the addresses in the first array is updated by its corresponding step value in the second array. These updated addresses are fed constantly into the multiplexer.

Select Counter

This is a counter that chooses which of the thirteen note addresses to send through the multiplexer to the wave generator lookup table. This is required for the circuit in order to actually choose which note to send through. Since the counter will cycle through all thirteen notes, it will allow for any and all of the notes to be played at once.

The counter receives an enable input from the sampler counter. When it does, it begins counting from zero to twelve, allowing the multiplexer to send in each updated note address to the lookup table. The counter then resets and waits for the next enable from the sample counter.

Note Multiplexer

This multiplexer chooses which note to send into the wave generator lookup table. This is required for the circuit in order to be able to generate multiple tones at once.

The multiplexer receives inputs to be multiplexed from the note address arrays. It also receives input from the select counter in the form of select bits. These bits tell the multiplexer which note address to allow past into the wave generator lookup table.

Wave Generator Lookup Table

This block generates a sine value based on the input it receives. This is required for the circuit in order to actually generate a sine wave which will be translated into sound.

This block was constructed by the core generator software in Xilinx, so we are not entirely sure of the mechanisms it uses. In general, though, the generator receives an address. It then indexes into a lookup table, finds the appropriate sine value, and outputs it.

Button Pressed Multiplexer

This multiplexer chooses whether to add the sine value to the accumulator based on whether the button for that note is being pressed. This is required for the circuit in order for the circuit to not always play all thirteen notes at once.

The multiplexer receives a single select bit from the keyboard input. If the button is pressed, it lets the sine value go through. Otherwise, it sends zero to the accumulator.

Accumulator

This block adds the sine values from the wave generator together. This is required for the circuit in order to play multiple notes at once. This idea is based on the theory of superposition (i.e. waves add directly to create superpositions of waves that act differently from either wave).

The accumulator receives input from the button pressed multiplexer. It adds this value to its stored value and saves it in a register when it receives a load input. When the terminal count is reached (all thirteen notes have cycled through), the accumulator is cleared to make room for the updated values.

Normalizer

This block normalizes the output of the accumulator. This is required for the circuit in order to play notes at a consistent volume no matter how many are pressed.

This block receives input from the accumulator and a load signal. Based on the number of buttons pressed (given by another input), the normalizer multiplies the accumulator input by a certain number, then outputs the first 12 bits of that number (equivalent to shifting the bits, or dividing by a power of two). This output is saved to a register and sent to the digital to analog converter.

Digital to Analog Converter

This block converts the digital signal to an analog signal that is fed into the output speaker to create the tones. This is required for the circuit in order to actually produce melodious tones.

This block was created by David Picard, so we are not entirely sure how the block functions. In general, however, it converts the full digital signal into a series of serial bits that are sent to the amplifier to produce the tones.

2.4 Construction and Debugging

We initially constructed note counters for each individual note. They were fed by a slow clock buffer than ran at 44.1kHz, and the note counters stepped by the necessary amount to generate the proper frequencies. We then created the multiplexer that would choose which note to feed into the wave generator lookup table and the select counter that would decide which note to multiplex in. Following this, we used the core generator to create the wave generator lookup table. We lastly implemented the ADDA converter that David Picard supplied to us and constructed a controller for the state machine. This design ultimately failed. We attempted to debug the system, but the system failed to output even a single note.

After some careful thought and discussion with Mitchell Goff, we changed our approach to the problem. We did away with the individual counters and instead used arrays to hold the addresses to the wave generator lookup table. Using a sampler counter, we updated the addresses of each note by the step specified in another array. We also moved the multiplexer system to the top module to simplify the design. This design approach worked, but we had an issue where the FPGA would only sound the high c. After some careful debugging and simulating, we realized that the latency in the wave generator lookup table was causing the circuit to exhibit undefined behavior. To remedy this, we created a slow clock to run all of the parts of the circuit except for the lookup table. By doing this, we effectively removed the latency from the table. We were then finally able to sound the correct notes, although we were not yet achieving polyphony.

The final step was adding in the accumulator and normalizer. The accumulator was constructed and worked without a hitch. However, when the normalizer was implemented, it would only work when the high c note was played. This problem was solved once we realized that we needed an extra state in our controller to allow the normalizer time to properly work. After adding an extra state to the controller, the circuit worked perfectly.

After achieving polyphony, we discussed extra features regarding the keyboard. Adding the suspension was a painless process with no debugging necessary. However, when we attempted to implement chord creation, there was simply not enough time to make it work properly, and so was scrapped.

3 Justification and Evaluation

Our initial solution to the polyphonic keyboard was ultimately scrapped in favor of a more sophisticated and simplistic design. While our initial solution may have worked had we figured out the bug in our code, the solution we ultimately adopted was far easier to understand, far easier to implement, and had the potential for far fewer bugs.

Our final design was straightforward and clear, even to those who did not work on our project. Its data flow is relatively simple given the complexity of the problem, and the combinational logic that it implements is abstracted in a way that generalizes it and allows the components to be used in other (possibly unrelated) projects. Other designs that we initially looked at (including our initial design) are clunky in terms of implementation, and rely far too much on data abstraction. While abstracting logic is good sometimes, it can also be deadly to a program/project if not correctly done. In the case of our final design, we took advantage of the fact that VHDL has the ability to synthesize arrays in hardware. This could be a flaw in our final design, as arrays may not always be present in hardware description languages, and so our project would not be portable. Ultimately, however, we believe that our design is the best possible for the problem we set out to solve.

If we were to have the opportunity to recreate the project, we would have gone over in more detail the goals of the project. Initially, while we understood what general ideas we needed to implement for this project to work, we did not discuss the various options for implementing these ideas. Had we done this, we believe that we would have realized the suitability of arrays for our design. In addition, we would have tried to abstract out our multiplexer. Although we had initially had it in a separate VHDL file, we chose to put it in the top module because we believed it to be a source of our bugs, and we chose not to move it back to its own file once we figured out where the actual bugs were originating. In this sense, the multiplexer would have also been abstracted and easily portable to other projects.

4 Conclusions

The goal of this project was to create a fully functional polyphonic keyboard. In other words, we set out to create an electronic that would be able to output multiple tones at once.

Originally, our proposal entailed multiple counters that would count independently of one another and update the notes. However, after our initial meeting with Professor Eric Hansen and David Picard, we realized that this design would not work with direct digital synthesis. After a fair number of iterations of our design, our final design was able to accomplish exactly what we specified in our proposal. In addition, we were able to add an extra feature that was not initially specified in our proposal.

For groups in the future who consider creating a polyphonic keyboard, our suggestion regarding its construction is to seriously think about the design before beginning to implement it. Ultimately, we scrapped about five or six hours worth of coding because we did not take an hour to sit down with the design and question its implementation. In addition, we would also caution future groups against trying to optimize sound quality at first. Although it would not be too difficult to optimize sound quality at the end of the project, we spent too much time attempting to get the best quality sound for our keyboard when we should have instead focused on simply getting the keyboard to sound at all.

All in all, our experience creating this keyboard was an overwhelmingly positive one. The students, TAs and professors who helped us on our design reaffirmed our faith in collaborative thinking. In addition, we learned much not only about digital electronics, but about our work habits as a team. We are very proud of our work and grateful to all those who made it possible.

5 Acknowledgements

We are grateful to Professor Eric Hansen, David Picard, and our TAs Hunter Black, Matthew West, Ellen Davenport, and Mac Keyser for their assistance during the term and for this project in particular. We would also like to thank our peers for their assistance in various parts of the conceptualization and debugging of our project. In particular, we would like to thank Dana Wieland and Mitchell Goff.

6 References

The note frequencies we generated were found on the Physics of Music - Notes page of Michigan Tech Department of Physics website.

URL: <http://www.phy.mtu.edu/suits/notefreqs.html>

7 Appendices

7.1 System Level Diagrams

1. Front Panel

 


Figure 1: This figure shows all relevant functional components of our polyphonic keyboard.

2. Functional Block Diagram

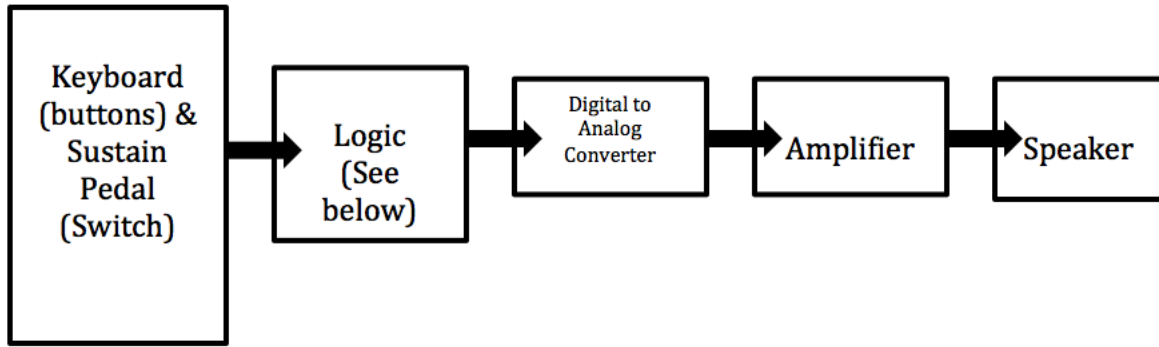


Figure 2: This figure shows the overall functional hardware block diagram. All elements were provided pmods, with the exception of the "Logic" box that is explored in the next figure.

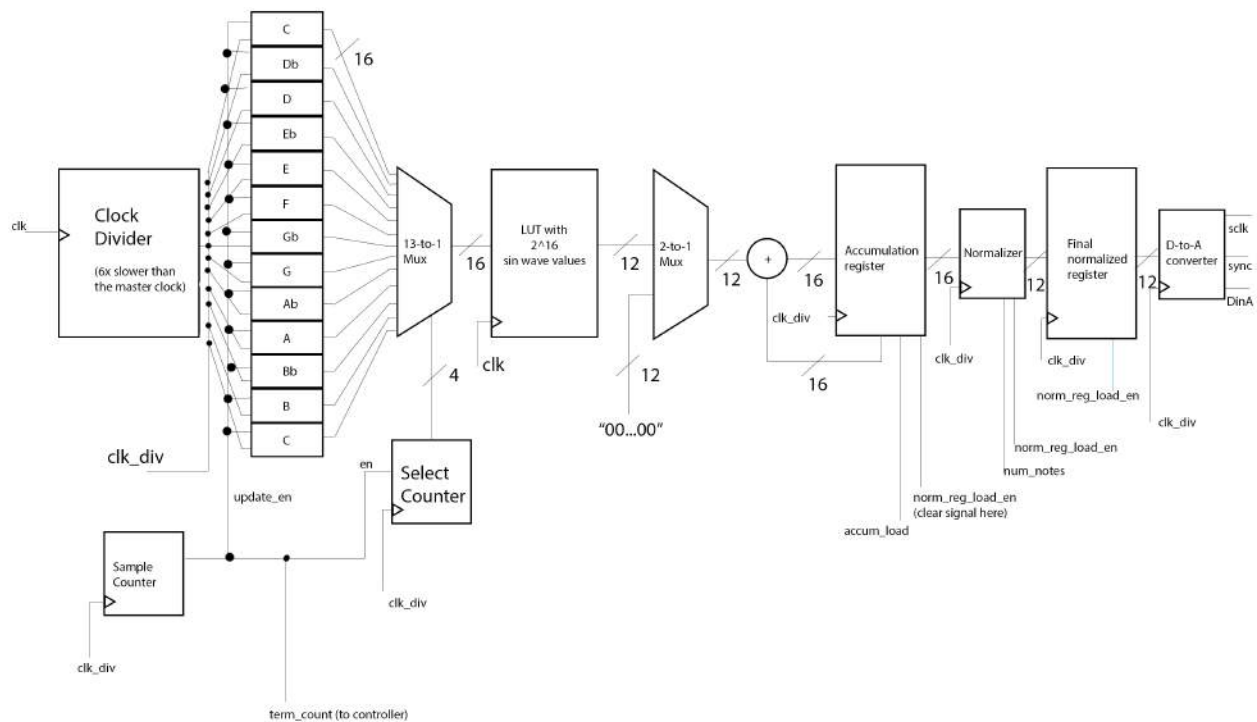


Figure 3: This figure shows the block diagram for the data path of our polyphonic keyboard.

3. **Schematic Diagram** Since we did not wire any off board components, there are no schematic diagrams

to be shown.

4. Package Map

 


Figure 4: This figure shows the port mappings for our polyphonic keyboard.

5. Parts List

| Reference | Quantity | Part Number | Description |
|-----------|----------|--------------|------------------------------------|
| Nexys3 | 1 | Nexys3 | Digilent Nexys3 board |
| ADC1 | 1 | 410-113 | Digilent Pmod-DA2 D/A converter |
| AMP | 1 | 410-233P-KIT | Digilent Pmod-AMP2 audio amplifier |
| BTN1-BTN4 | 4 | 410-077P | Digilent Pmod-BTN 4-button module |
| SPKR | 1 | | Speaker |

Table 1: Parts needed to create our keyboard.

7.2 Programmed Logic

1. State Diagrams

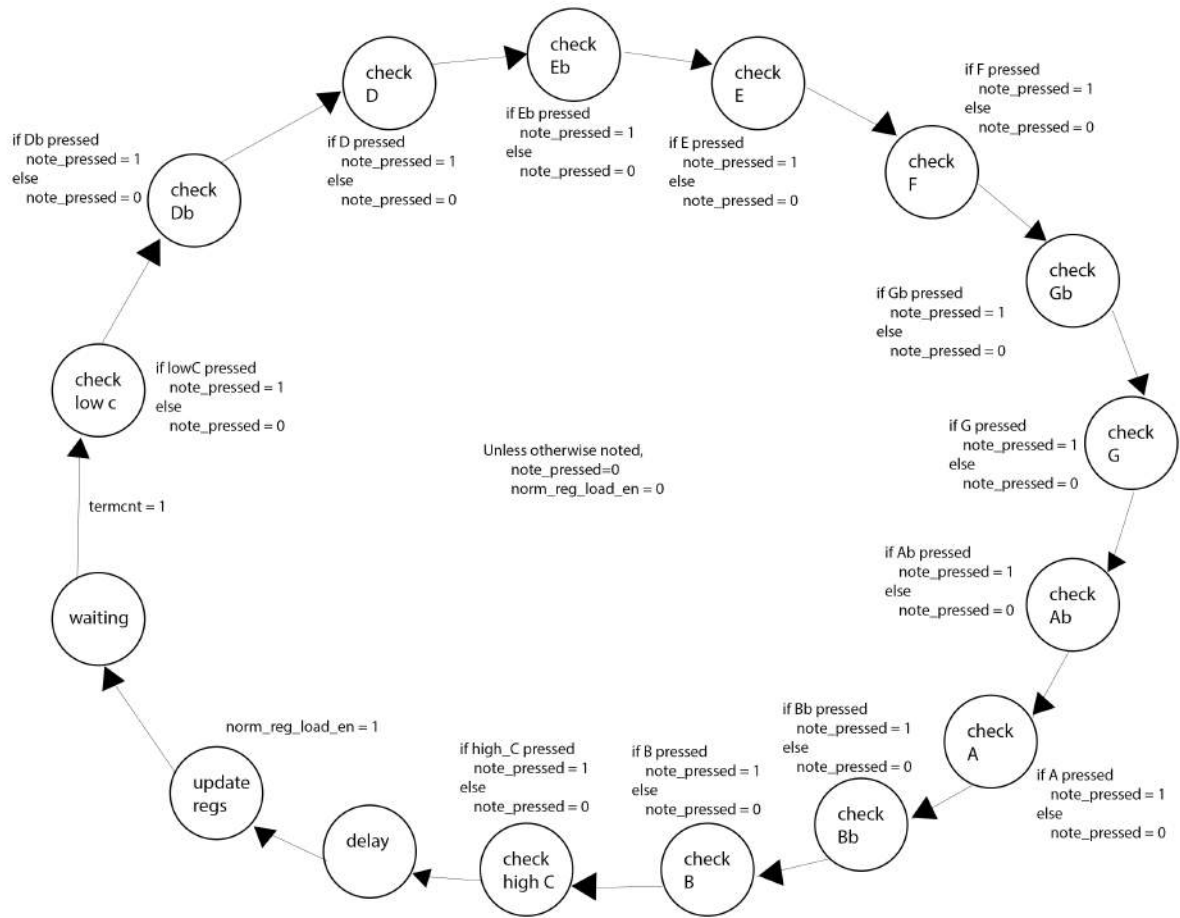


Figure 5: This figure shows the state machine used by our Keyboard Controller module to control the datapath for the polyphonic keyboard.

2. VHDL Code

Keyboard Top Module:

```
1      --
2      -----
3      -- Company: ENGS 31 15X
4      -- Engineer: Liane Makatura and Stylianos Tegas
5      --
6      -- Create Date:    20:33:50 08/19/2015
7      -- Design Name:
8      -- Module Name:    KeyboardTop - Behavioral
9      -- Project Name:
10     -- Target Devices:
11     -- Tool versions:
12     -- Description:
13     --
14     -- Dependencies:
15     --
16     -- Revision:
17     -- Revision 0.01 - File Created
18     -- Additional Comments:
19     --
20     -----
21     library IEEE;
22     use IEEE.STD_LOGIC_1164.ALL;
23
24     -- Uncomment the following library declaration if using
25     -- arithmetic functions with Signed or Unsigned values
26     use IEEE.NUMERIC_STD.ALL;
27
28     -- Uncomment the following library declaration if instantiating
29     -- any Xilinx primitives in this code.
30     --library UNISIM;
31     --use UNISIM.VComponents.all;
32
33     entity KeyboardTop is
34         Port ( clk : in  STD_LOGIC;
35               noteb : in STD_LOGIC_VECTOR (12 downto 0);
36               sus : in  STD_LOGIC;
37               sync : out STD_LOGIC;
38               sclk : out STD_LOGIC;
39               DinA : out STD_LOGIC);
40     end KeyboardTop;
41
42     architecture Behavioral of KeyboardTop is
43         type wave_counter_dt is array (12 downto 0) of unsigned (15 downto 0);
44
45         --constants
46         constant note_steps : wave_counter_dt := (to_unsigned(389, 16), -- c
47                                                    to_unsigned(412, 16), -- dflat
48                                                    to_unsigned(436, 16), -- d
49                                                    to_unsigned(462, 16), -- eflat
50                                                    to_unsigned(490, 16), -- e
51                                                    to_unsigned(519, 16), -- f
52                                                    to_unsigned(550, 16), -- gflat
53                                                    to_unsigned(583, 16), -- g
54                                                    to_unsigned(617, 16), -- aflat
55                                                    to_unsigned(654, 16), -- a
56                                                    to_unsigned(693, 16), -- bflat
57                                                    to_unsigned(734, 16), -- b
58                                                    to_unsigned(778, 16) -- c
59                                                    );
60
61         --signals
```



```

63 signal inotes: std_logic_vector(12 downto 0) := noteb;
signal clk_div: std_logic := '0'; --clock divider
signal select_en: std_logic := '0'; --enables checking of buttons
65 signal note_pressed: std_logic := '0'; --checks whether button is pressed

67 signal selectbits: std_logic_vector (3 downto 0) := (others => '0'); --holds select bits
    for the multiplexer
signal accum_load: std_logic := '0'; --allows accumulator to load
69 signal load: std_logic := '0'; --allows normalizer to load

71 --addresses for each of the notes, sent to the mux
signal note_addresses : wave_counter_dt := (others => (others => '0')); -- initialize all
    addresses to 0

73 signal noteadd: std_logic_vector (15 downto 0) := (others => '0'); --address for the
    correct note to send to lut
75 signal note_to_add: std_logic_vector (11 downto 0) := (others => '0'); --value of the
    sine wave to add to accumulator
signal sum_note: std_logic_vector (15 downto 0) := (others => '0'); --the summed values
    of the sine wave for polyphony
77 signal num_notes: std_logic_vector (3 downto 0) := (others => '0'); -- how many notes
    are pressed, for normalization
signal final_note: std_logic_vector (11 downto 0) := (others => '0'); --the normalized
    note to be sent to the adda converter

79 --components
81 -- clock divider for the datapath
-- brings it down to a clock 6 times slower than the master
83 COMPONENT ClockDivider
PORT(
85     clk : IN std_logic;
        clk_div : OUT std_logic
87 );
END COMPONENT;

89 -- sampler counter for address updating and cycling
91 COMPONENT SamplerCounter
PORT(
93     clk : IN std_logic;
        term_cnt : OUT std_logic
95 );
END COMPONENT;

97 -- select counter for the mux, to loop through all notes
99 COMPONENT SelectCounter
PORT(
101     clk : IN std_logic;
        en : IN std_logic;
103     selectbits : OUT std_logic_vector(3 downto 0)
    );
105 END COMPONENT;

107 -- digital to analog converter
109 COMPONENT adda
PORT(
111     clk : IN std_logic;
        tone : IN std_logic_vector(11 downto 0);
        sync : OUT std_logic;
113     DinA : OUT std_logic;
        sclk : OUT std_logic
115 );
END COMPONENT;

117 -- LUT for sin values
119 COMPONENT WaveGen

```

```

121     PORT (
122         clk : IN STD_LOGIC;
123         phase_in : IN STD_LOGIC_VECTOR(15 downto 0);
124         sine : OUT STD_LOGIC_VECTOR(11 DOWNT0 0)
125     );
126 END COMPONENT;
127
128 --controller for data path
129 COMPONENT KeyboardController
130 PORT(
131     clk : IN std_logic;
132     noteb : IN std_logic_vector (12 downto 0);
133     termcnt : IN std_logic;
134     note_pressed : OUT std_logic;
135     norm_reg_load_en : OUT std_logic
136 );
137 END COMPONENT;
138
139 -- accumulates the sin values for polyphony
140 COMPONENT Accumulator
141 PORT(
142     clk : IN std_logic;
143     note_to_add : IN std_logic_vector(11 downto 0);
144     load_en : IN std_logic;
145     clear_en : IN std_logic;
146     note_to_norm : OUT std_logic_vector(15 downto 0)
147 );
148 END COMPONENT;
149
150 -- normalizes the accumulated value by the number of notes played to get the final output
151 -- same volume no matter how many notes are being played
152 COMPONENT Normalizer
153 PORT(
154     clk : IN std_logic;
155     load_en : IN std_logic;
156     note_to_norm : IN std_logic_vector(15 downto 0);
157     num_note : IN std_logic_vector(3 downto 0);
158     final_note : OUT std_logic_vector(11 downto 0)
159 );
160 END COMPONENT;
161
162 begin
163
164 --processes
165
166 --creates suspension
167 suspension: process(clk_div)
168 begin
169
170     if rising_edge(clk_div) then
171         inotes <= inotes;
172         if sus = '1' then
173             for n in 0 to 12 loop
174                 if noteb(n) = '1' then
175                     inotes(n) <= '1';
176                 else
177                     inotes(n) <= inotes(n);
178                 end if;
179             end loop;
180         else
181             inotes <= noteb;
182         end if;
183     end if;

```

```

185 end process;

187 -- updates all the note addresses
address_update: process(clk_div)
189 begin

191     if rising_edge(clk_div) then
192         if select_en = '1' then
193             for n in 0 to 12 loop
194                 note_addresses(n) <= note_addresses(n) + note_steps(n);
195             end loop;
196         end if;
197     end if;

199 end process;

201 -- determines which address to retrieve from the sine LUT
address_mux: process(selectbits, note_addresses)
203 begin

205     case selectbits is
206         when "0000" =>
207             noteadd <= std_logic_vector(note_addresses(12));
208         when "0001" =>
209             noteadd <= std_logic_vector(note_addresses(11));
210         when "0010" =>
211             noteadd <= std_logic_vector(note_addresses(10));
212         when "0011" =>
213             noteadd <= std_logic_vector(note_addresses(9));
214         when "0100" =>
215             noteadd <= std_logic_vector(note_addresses(8));
216         when "0101" =>
217             noteadd <= std_logic_vector(note_addresses(7));
218         when "0110" =>
219             noteadd <= std_logic_vector(note_addresses(6));
220         when "0111" =>
221             noteadd <= std_logic_vector(note_addresses(5));
222         when "1000" =>
223             noteadd <= std_logic_vector(note_addresses(4));
224         when "1001" =>
225             noteadd <= std_logic_vector(note_addresses(3));
226         when "1010" =>
227             noteadd <= std_logic_vector(note_addresses(2));
228         when "1011" =>
229             noteadd <= std_logic_vector(note_addresses(1));
230         when "1100" =>
231             noteadd <= std_logic_vector(note_addresses(0));
232         when others =>
233             noteadd <= "0000000000000000";
234     end case;

235 end process;

237 --checks if the note address should go through to accumulator and adds to number of note
    pressed for normalizer
239 tonemux: process(note_pressed)
241 begin

242     if note_pressed = '1' then
243         accum_load <= '1';
244     else
245         accum_load <= '0';
246     end if;

247 end process;

```

```

249 -- keeps track of how many notes are being played
251 num_note_reg: process(clk_div)
252 begin
253     if rising_edge(clk_div) then
254         num_notes <= num_notes;
255         if note_pressed = '1' then
256             num_notes <= std_logic_vector(unsigned(num_notes) + 1);
257         elsif select_en <= '1' then
258             num_notes <= "0000";
259         end if;
260     end if;
261 end process;
262
263 end process;
264
265 --portmaps
266
267 -- clock divider for the wave counters
268 -- brings it down to a 1024Hz clock
269 Inst_ClockDivider: ClockDivider PORT MAP (
270     clk => clk,
271     clk_div => clk_div
272 );
273
274 -- Counter for sampling rate, outputs tc when it's time to sample
275 Inst_SamplerCounter: SamplerCounter PORT MAP (
276     clk => clk_div,
277     term_cnt => select_en
278 );
279
280 -- select counter for the mux, to loop through all notes
281 Inst_SelectCounter: SelectCounter PORT MAP (
282     clk => clk_div,
283     en => select_en,
284     selectbits => selectbits
285 );
286
287 -- LUT for sin values
288 Sine_LUT : WaveGen
289 PORT MAP (
290     clk => clk,
291     phase_in => noteadd,
292     sine => note_to_add
293 );
294
295 -- digital to analog converter
296 Inst_adda: adda PORT MAP (
297     clk => clk,
298     tone => final_note,
299     sync => sync,
300     DinA => DinA,
301     sclk => sclk
302 );
303
304 --Controller for datapath
305 Inst_KeyboardController: KeyboardController PORT MAP (
306     clk => clk_div,
307     noteb => inotes,
308     termcnt => select_en,
309     note_pressed => note_pressed,
310     norm_reg_load_en => load
311 );
312
313 -- accumulator for polyphony

```

```

315 Inst_Accumulator: Accumulator PORT MAP(
    clk => clk_div,
    note_to_add => note_to_add,
317 load_en => accum_load,
    clear_en => load,
319 note_to_norm => sum_note
);
321
-- normalizes the accumulated value by the number of notes being played
323 Inst_Normalizer: Normalizer PORT MAP(
    clk => clk_div,
325 load_en => load,
    note_to_norm => sum_note,
327 num_note => num_notes,
    final_note => final_note
329 );
331
end Behavioral;
333
335

```

Keyboard Controller:

```
1      --
2      -----
3      -- Company: ENGS 31 15X
4      -- Engineer: Stylianos Tegas and Liane Makatura
5      --
6      -- Create Date:      22:00:52 08/19/2015
7      -- Design Name:
8      -- Module Name:      KeyboardController - Behavioral
9      -- Project Name:
10     -- Target Devices:
11     -- Tool versions:
12     -- Description:
13     --
14     -- Dependencies:
15     --
16     -- Revision:
17     -- Revision 0.01 - File Created
18     -- Additional Comments:
19     --
20     -----
21     library IEEE;
22     use IEEE.STD_LOGIC_1164.ALL;
23
24     -- Uncomment the following library declaration if using
25     -- arithmetic functions with Signed or Unsigned values
26     use IEEE.NUMERIC_STD.ALL;
27
28     -- Uncomment the following library declaration if instantiating
29     -- any Xilinx primitives in this code.
30     --library UNISIM;
31     ----use UNISIM.VComponents.all;
32
33     entity KeyboardController is
34         Port ( clk : in  STD_LOGIC;
35               noteb : in  STD_LOGIC_VECTOR (12 downto 0);
36               termcnt : in  STD_LOGIC;
37               note_pressed : out  STD_LOGIC;
38               norm_reg_load_en : out  STD_LOGIC);
39     end KeyboardController;
40
41     architecture Behavioral of KeyboardController is
42         type state_type is (check_lowc, check_dflat, check_d, check_eflat, check_e,
43                             check_f, check_gflat, check_g, check_aflat, check_a,
44                             check_bflat, check_b, check_highc, update_regs, waiting, delay);
45         signal state, next_state : state_type := check_lowc;
46
47     begin
48
49         control: process(state, noteb, termcnt)
50         begin
51
52             note_pressed <= '0'; --defaults
53             norm_reg_load_en <= '0';
54             next_state <= state;
55
56             case state is
57                 when check_lowc =>
58                     if noteb(12) = '1' then -- if low C is pressed, let the mux know
59                         note_pressed <= '1';
60                     end if;
61                     next_state <= check_dflat;
62                 when check_dflat =>
```

| | | |
|---|---|---|
| 63 65 67 69 71 73 75 77 79 81 83 85 87 89 91 93 95 97 99 101 103 105 107 109 111 113 115 117 119 121 123 125 | <pre> if noteb(11) = '1' then note_pressed <= '1'; end if; next_state <= check_d; when check_d => if noteb(10) = '1' then note_pressed <= '1'; end if; next_state <= check_eflat; when check_eflat => if noteb(9) = '1' then note_pressed <= '1'; end if; next_state <= check_e; when check_e => if noteb(8) = '1' then note_pressed <= '1'; end if; next_state <= check_f; when check_f => if noteb(7) = '1' then note_pressed <= '1'; end if; next_state <= check_gflat; when check_gflat => if noteb(6) = '1' then note_pressed <= '1'; end if; next_state <= check_g; when check_g => if noteb(5) = '1' then note_pressed <= '1'; end if; next_state <= check_aflat; when check_aflat => if noteb(4) = '1' then note_pressed <= '1'; end if; next_state <= check_a; when check_a => if noteb(3) = '1' then note_pressed <= '1'; end if; next_state <= check_bflat; when check_bflat => if noteb(2) = '1' then note_pressed <= '1'; end if; next_state <= check_b; when check_b => if noteb(1) = '1' then note_pressed <= '1'; end if; next_state <= check_highc; when check_highc => if noteb(0) = '1' then note_pressed <= '1'; end if; next_state <= delay; when update_regs => norm_reg_load_en <= '1'; second register next_state <= waiting; when waiting => if termcnt = '1' then </pre> | <pre> -- if Db is pressed, let the mux know -- if D is pressed, let the mux know -- if Eb is pressed, let the mux know -- if E is pressed, let the mux know -- if F is pressed, let the mux know -- if Gb is pressed, let the mux know -- if G is pressed, let the mux know -- if Ab is pressed, let the mux know -- if A is pressed, let the mux know -- if Bb is pressed, let the mux know -- if B is pressed, let the mux know -- if high C is pressed, let the mux know -- load in the normalized value to the -- start checking again -- delay until next sampling time </pre> |
|---|---|---|

```

127         next_state <= check_lowc;
128     end if;
129     when delay => -- gives time for normalization on high c
130         next_state <= update_regs;
131     end case;
132 end process;
133
134
135 update_state: process(clk)
136 begin
137     if rising_edge(clk) then
138         state <= next_state;
139     end if;
140 end process;
141
142 end Behavioral;
143
144
145

```


Clock Divider:

```
--  
-----  
2      -- Company: ENGS 31 15X  
3      -- Engineer: Stylianos Tegas and Liane Makatura  
4      --  
5      -- Create Date:      20:14:08 08/19/2015  
6      -- Design Name:  
7      -- Module Name:      ClockDivider - Behavioral  
8      -- Project Name:  
9      -- Target Devices:  
10     -- Tool versions:  
11     -- Description:  
12     --  
13     -- Dependencies:  
14     --  
15     -- Revision:  
16     -- Revision 0.01 - File Created  
17     -- Additional Comments:  
18     --  
19     --  
20     -----  
21     library IEEE;  
22     use IEEE.STD_LOGIC_1164.ALL;  
23  
24     -- Uncomment the following library declaration if using  
25     -- arithmetic functions with Signed or Unsigned values  
26     use IEEE.NUMERIC_STD.ALL;  
27  
28     -- Uncomment the following library declaration if instantiating  
29     -- any Xilinx primitives in this code.  
30     --library UNISIM;  
31     --use UNISIM.VComponents.all;  
32  
33     entity ClockDivider is  
34         Port ( clk : in  STD_LOGIC;  
35               clk_div : out STD_LOGIC);  
36     end ClockDivider;  
37  
38     architecture Behavioral of ClockDivider is  
39         constant clk_div_value: integer := 3;  
40         signal count: unsigned (1 downto 0) := (others => '0');  
41         signal tog: std_logic := '0';  
42         begin  
43  
44         divider: process(clk)  
45         begin  
46  
47             if rising_edge(clk) then  
48                 if count = (clk_div_value - 1) then  
49                     tog <= NOT(tog);      -- toggle the clock value  
50                     count <= (others => '0');  
51                 else  
52                     count <= count + 1;  
53                 end if;  
54             end if;  
55  
56         end process;  
57  
58         clk_div <= tog;      -- assign the output  
59  
60     end Behavioral;
```

Select Counter:

```
1      --
2      -----
3      -- Company: ENGS 31 15X
4      -- Engineer: Stylianos Tegas and Liane Makatura
5      --
6      -- Create Date:      20:09:36 08/19/2015
7      -- Design Name:
8      -- Module Name:      SelectCounter - Behavioral
9      -- Project Name:
10     -- Target Devices:
11     -- Tool versions:
12     -- Description:
13     --
14     -- Dependencies:
15     --
16     -- Revision:
17     -- Revision 0.01 - File Created
18     -- Additional Comments:
19     --
20     -----
21     library IEEE;
22     use IEEE.STD_LOGIC_1164.ALL;
23
24     -- Uncomment the following library declaration if using
25     -- arithmetic functions with Signed or Unsigned values
26     use IEEE.NUMERIC_STD.ALL;
27
28     -- Uncomment the following library declaration if instantiating
29     -- any Xilinx primitives in this code.
30     --library UNISIM;
31     --use UNISIM.VComponents.all;
32
33     entity SelectCounter is
34         Port ( clk : in  STD_LOGIC;
35               en  : in  STD_LOGIC;
36               selectbits : out STD_LOGIC_VECTOR (3 downto 0));
37     end SelectCounter;
38
39     architecture Behavioral of SelectCounter is
40         signal iQ: unsigned (3 downto 0) := "1100";
41     begin
42
43         count: process(clk)
44         begin
45
46             if rising_edge(clk) then
47
48                 if en = '1' AND iQ = "1100" then          --if enable is high and iQ has
reached terminal count, reset
49                     iQ <= "0000";
50                     elsif iQ >= "0000" AND iQ < "1100" then  --if iQ in process of counting,
continue
51                         iQ <= iQ + 1;
52                     else                                     --if done counting but enable is not high,
feed 12
53                         iQ <= "1100";
54                     end if;
55             end if;
56         end process;
57     end architecture;
```

```
55         end if;
57     end process;
59     selectbits <= std_logic_vector(iQ);      --assign select bits
61     end Behavioral;
63
```

Accumulator:

```
1      --
2      -----
3      -- Company: ENGS 31 15X
4      -- Engineer: Stylianos Tegas and Liane Makatura
5      --
6      -- Create Date:      13:57:27 08/22/2015
7      -- Design Name:
8      -- Module Name:      Accumulator - Behavioral
9      -- Project Name:
10     -- Target Devices:
11     -- Tool versions:
12     -- Description:
13     --
14     -- Dependencies:
15     --
16     -- Revision:
17     -- Revision 0.01 - File Created
18     -- Additional Comments:
19     --
20     -----
21     library IEEE;
22     use IEEE.STD_LOGIC_1164.ALL;
23
24     -- Uncomment the following library declaration if using
25     -- arithmetic functions with Signed or Unsigned values
26     use IEEE.NUMERIC_STD.ALL;
27
28     -- Uncomment the following library declaration if instantiating
29     -- any Xilinx primitives in this code.
30     --library UNISIM;
31     --use UNISIM.VComponents.all;
32
33     entity Accumulator is
34         Port ( clk : in STD_LOGIC;
35               note_to_add : in STD_LOGIC_VECTOR (11 downto 0);
36               load_en : in STD_LOGIC;
37               clear_en : in STD_LOGIC;
38               note_to_norm : out STD_LOGIC_VECTOR (15 downto 0));
39     end Accumulator;
40
41     architecture Behavioral of Accumulator is
42         signal summed_note: std_logic_vector (15 downto 0) := (others => '0');
43
44     begin
45
46         accumulate: process(clk)
47         begin
48
49             if rising_edge(clk) then
50                 summed_note <= summed_note;           -- accumulate the sin waves
51                 if clear_en = '1' then                -- if clear then clear register
52                     summed_note <= (others => '0');
53                 elsif load_en = '1' then              -- if load load new signal
54                     summed_note <= std_logic_vector(unsigned(summed_note) + unsigned(
55 note_to_add));
56                     end if;
57                 end if;
58
59             end process;
60
61             note_to_norm <= summed_note;
```

61

```
end Behavioral;
```

Normalizer:

```
1      --
2      -----
3      -- Company: ENGS 31 15X
4      -- Engineer: Stylianos Tegas and Liane Makatura
5      --
6      -- Create Date:      14:36:20 08/22/2015
7      -- Design Name:
8      -- Module Name:      Normalizer - Behavioral
9      -- Project Name:
10     -- Target Devices:
11     -- Tool versions:
12     -- Description:
13     --
14     -- Dependencies:
15     --
16     -- Revision:
17     -- Revision 0.01 - File Created
18     -- Additional Comments:
19     --
20     -----
21     library IEEE;
22     use IEEE.STD_LOGIC_1164.ALL;
23
24     -- Uncomment the following library declaration if using
25     -- arithmetic functions with Signed or Unsigned values
26     use IEEE.NUMERIC_STD.ALL;
27
28     -- Uncomment the following library declaration if instantiating
29     -- any Xilinx primitives in this code.
30     --library UNISIM;
31     --use UNISIM.VComponents.all;
32
33     entity Normalizer is
34         Port ( clk : in STD_LOGIC;
35               load_en : in STD_LOGIC;
36               note_to_norm : in STD_LOGIC_VECTOR (15 downto 0);
37               num_note : in STD_LOGIC_VECTOR (3 downto 0);
38               final_note : out STD_LOGIC_VECTOR (11 downto 0));
39     end Normalizer;
40
41     architecture Behavioral of Normalizer is
42         type array_dt is array (12 downto 0) of unsigned (11 downto 0);
43         constant mult_factors : array_dt := (to_unsigned(4095, 12), -- 1 note
44                                               to_unsigned(2896, 12), -- 2 notes
45                                               to_unsigned(2365, 12), -- 3 notes
46                                               to_unsigned(2048, 12), -- 4 notes
47                                               to_unsigned(1832, 12), -- 5 notes
48                                               to_unsigned(1672, 12), -- 6 notes
49                                               to_unsigned(1548, 12), -- 7 notes
50                                               to_unsigned(1448, 12), -- 8 notes
51                                               to_unsigned(1365, 12), -- 9 notes
52                                               to_unsigned(1295, 12), -- 10 notes
53                                               to_unsigned(1235, 12), -- 11 notes
54                                               to_unsigned(1182, 12), -- 12 notes
55                                               to_unsigned(1136, 12) -- 13 notes
56                                               );
57         signal multi_note: std_logic_vector (27 downto 0) := (others => '0');
58         signal iQ: std_logic_vector (11 downto 0) := (others => '0');
59
60     begin
61
62         normalize: process(note_to_norm, num_note)
```

```

63         begin
64             if num_note = "0000" then          -- prevents indexing out of bounds
65                 multi_note <= std_logic_vector(unsigned(note_to_norm) * mult_factors(
to_integer(unsigned(num_note))));
66             else
67                 multi_note <= std_logic_vector(unsigned(note_to_norm) * mult_factors(
to_integer(unsigned(num_note)-1)));
68             end if;
69
70         end process;
71
72         load: process(clk)
73         begin
74
75             if rising_edge(clk) then
76                 if load_en = '1' then
77                     iQ <= multi_note(27 downto 16); --take first 12 bits
78                 else
79                     iQ <= iQ;
80                 end if;
81             end if;
82
83         end process;
84
85         final_note <= iQ;
86
87     end Behavioral;
88
89

```

Adda Converter:

```
1      --
2      -----
3      -- Company: Dartmouth College
4      -- Engineer: David Picard
5      -- Modified by Stylianos Tegas and Liane Makatura
6      -- Final Project: ENGS 31 15X
7      --
8      -- Create Date: 04/29/2015 02:32:19 PM
9      -- Design Name:
10     -- Module Name: adda - Behavioral
11     -- Project Name:
12     -- Target Devices:
13     -- Tool Versions:
14     -- Description:
15     --
16     -- Dependencies:
17     --
18     -- Revision:
19     -- Revision 0.01 - File Created
20     -- Additional Comments:
21     --
22     -----
23
24     library IEEE;
25     use IEEE.STD_LOGIC_1164.ALL;
26     use IEEE.numeric_std.ALL; -- needed for arithmetic
27
28     library UNISIM; -- needed for the BUFG component
29     use UNISIM.Vcomponents.ALL;
30
31     entity adda is
32     Port (
33         clk : in STD_LOGIC;
34         tone : in STD_LOGIC_VECTOR (11 downto 0);
35         sync : out std_logic;
36         DinA : out std_logic;
37         sclk : out std_logic
38     );
39     end adda;
40
41     architecture Behavioral of adda is
42
43
44
45
46     signal lastsampleclk : STD_LOGIC;
47     signal sampleclk : STD_LOGIC := '0';
48
49     signal den_in : STD_LOGIC;
50     signal dwe_in : std_logic;
51     signal di_in : STD_LOGIC_VECTOR(15 downto 0);
52     signal daddr_in : std_LOGIC_vector(6 downto 0);
53     signal sampledvalue : STD_LOGIC_VECTOR(15 downto 0) := x"1234";
54     signal sampledvalue2 : STD_LOGIC_VECTOR(15 downto 0) := x"5555";
55     signal DATA1 : STD_LOGIC_VECTOR(15 downto 0) := x"2345";
56     signal DATA2 : STD_LOGIC_VECTOR(15 downto 0) := x"3456";
57     signal busy, DONE, nSYNC, START : STD_LOGIC;
58     constant control : std_logic_vector(3 downto 0) := "0000";
59
60     type states is (Idle, ShiftOut, SyncData);
61     signal current_state : states;
```



```

63     signal next_state      : states;
65
66     signal temp1           : std_logic_vector(15 downto 0);
67     signal clk_div         : std_logic;
68     signal clk_counter     : unsigned(27 downto 0) := x"0000000";
69     signal shiftCounter    : unsigned(4 downto 0);
70     signal enShiftCounter  : std_logic;
71     signal enParalelLoad   : std_logic;
72     signal clk_counter2    : integer := 0;
73     signal clk_en          : std_logic := '0';
74     signal data_counter    : unsigned (4 downto 0) := "00000";
75     signal data_counter2   : unsigned (11 downto 0) := x"000";
76
77     begin
78
79         sclk <= clk_en;
80
81         Slow_clock_buffer: BUFG
82             port map (I => clk_en,
83                     O => sampleclk );
84
85         -----
86
87         clock_divide2 : process(clk)
88         begin
89             if (clk = '1' and clk'event) then
90                 if clk_counter2 = 5 then clk_en <= not clk_en;
91                     clk_counter2 <= 0;
92                 else clk_counter2 <= clk_counter2 + 1;
93             end if;
94         end process;
95         -----
96
97         count_bits : process (sampleclk)
98         begin
99             if (sampleclk'event) and (sampleclk = '1') then
100                 start <= '0';
101                 if data_counter = "11001" then data_counter <= (others => '0');
102                     start <= '1';
103                 else data_counter <= data_counter + 1;
104             end if;
105
106             end if; --clk
107         end process;
108
109         -----
110
111         counter : process(sampleclk)
112         begin
113             if (sampleclk = '1' and sampleclk'event) then
114                 DinA <= temp1(15);
115                 if start = '1' then
116                     temp1 <= "0000" & not(tone(11)) & tone(10 downto 0);
117                 end if;
118                 if enParalelLoad = '1' then
119                     shiftCounter <= "00000";
120
121                 elsif (enShiftCounter = '1') then
122                     temp1 <= temp1(14 downto 0)&temp1(15);
123                     shiftCounter <= shiftCounter + 1;

```

```

125         end if;
126         end if;
127     end process;

128
129     --
-----
130
131     SYNC_PROC: process (sampleclk)
132     begin
133         if (sampleclk'event and sampleclk = '1') then
134             current_state <= next_state;
135             sync <= nsync;
136         end if;
137     end process;

138
139     --
-----
140
141     OUTPUT_DECODE: process (current_state)
142     begin
143         if current_state = Idle then
144             enShiftCounter <= '0';
145             nSYNC <= '1';
146             enParalelLoad <= '1';
147         elsif current_state = ShiftOut then
148             enShiftCounter <= '1';
149             nSYNC <= '0';
150             enParalelLoad <= '0';
151         else --if current_state = SyncData then
152             enShiftCounter <= '0';
153             nSYNC <= '1';
154             enParalelLoad <= '0';
155         end if;
156     end process;

157
158     --
-----
159
160     NEXT_STATE_DECODE: process (current_state, START, shiftCounter)
161     begin
162
163         next_state <= current_state;

164
165         case (current_state) is
166             when Idle =>
167                 if START = '1' then
168                     next_state <= ShiftOut;
169                 end if;
170             when ShiftOut =>
171                 if shiftCounter = "01111" then --"10000" then
172                     next_state <= SyncData;
173                 end if;
174             when SyncData =>
175                 if START = '0' then
176                     next_state <= Idle;
177                 end if;
178             when others =>
179                 next_state <= Idle;
180         end case;
181     end process;

182
183     end Behavioral;
184
185

```

UCF:

```
## This file is a general .ucf for Nexys3 rev B board
## To use it in a project:
## - remove or comment the lines corresponding to unused pins
## - rename the used signals according to the project

## Clock signal
NET "clk" LOC = "V10" | IOSTANDARD = "LVCMOS33"; #Bank = 2, pin name =
    IO_L30N_GCLK0_USERCCLK, Sch name = GCLK
Net "clk" TNM_NET = sys_clk_pin;
TIMESPEC TS_sys_clk_pin = PERIOD sys_clk_pin 100000 kHz;
PIN "Inst_adda/Slow_clock_buffer.0" CLOCK_DEDICATED_ROUTE = FALSE;

## 7 segment display
#NET "seg<0>" LOC = "T17" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L51P_M1DQ12, Sch name = CA
#NET "seg<1>" LOC = "T18" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L51N_M1DQ13, Sch name = CB
#NET "seg<2>" LOC = "U17" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L52P_M1DQ14, Sch name = CC
#NET "seg<3>" LOC = "U18" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L52N_M1DQ15, Sch name = CD
#NET "seg<4>" LOC = "M14" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name = IO_L53P
    , Sch name = CE
#NET "seg<5>" LOC = "N14" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L53N_VREF, Sch name = CF
#NET "seg<6>" LOC = "L14" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name = IO_L61P
    , Sch name = CG
#NET "seg<7>" LOC = "M13" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name = IO_L61N
    , Sch name = DP

#NET "an<0>" LOC = "N16" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L50N_M1UDQSN, Sch name = AN0
#NET "an<1>" LOC = "N15" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L50P_M1UDQS, Sch name = AN1
#NET "an<2>" LOC = "P18" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L49N_M1DQ11, Sch name = AN2
#NET "an<3>" LOC = "P17" | IOSTANDARD = "LVCMOS33"; #Bank = 1, Pin name =
    IO_L49P_M1DQ10, Sch name = AN3

## Leds
#NET "Led<0>" LOC = "U16" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
    IO_L2P_CMPCLK, Sch name = LD0
#NET "Led<1>" LOC = "V16" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
    IO_L2N_CMPMOSI, Sch name = LD1
#NET "Led<2>" LOC = "U15" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L5P,
    Sch name = LD2
#NET "Led<3>" LOC = "V15" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L5N,
    Sch name = LD3
#NET "Led<4>" LOC = "M11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L15P
    , Sch name = LD4
#NET "Led<5>" LOC = "N11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L15N
    , Sch name = LD5
#NET "Led<6>" LOC = "R11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L16P
    , Sch name = LD6
#NET "Led<7>" LOC = "T11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
    IO_L16N_VREF, Sch name = LD7

## Switches
NET "sus" LOC = "T10" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
    IO_L29N_GCLK2, Sch name = SW0
#NET "dflatb" LOC = "T9" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
```

```

IO_L32P_GCLK29,          Sch name = SW1
42 #NET "db"              LOC = "V9" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
IO_L32N_GCLK28,          Sch name = SW2
#NET "eflatb"            LOC = "M8" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
IO_L40P,                 Sch name = SW3
44 #NET "maj"             LOC = "N8" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L40N,
Sch name = SW4
#NET "min"               LOC = "U8" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L41P,
Sch name = SW5
46 #NET "dim"             LOC = "V8" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
IO_L41N_VREF,            Sch name = SW6
#NET "aug"               LOC = "T5" | IOSTANDARD = "LVCMOS33"; #Bank = MISC, Pin name =
IO_L48N_RDWR_B_VREF_2,   Sch name = SW7
48
50 ## Buttons
#NET "aflatb"            LOC = "B8" | IOSTANDARD = "LVCMOS33"; #Bank = 0, Pin name = IO_L33P
,                          Sch name = BTNS
52 #NET "maj"             LOC = "A8" | IOSTANDARD = "LVCMOS33"; #Bank = 0, Pin name = IO_L33N,
Sch name = BTNU
#NET "dim"               LOC = "C4" | IOSTANDARD = "LVCMOS33"; #Bank = 0, Pin name =
IO_L1N_VREF,             Sch name = BTNL
54 #NET "min"             LOC = "C9" | IOSTANDARD = "LVCMOS33"; #Bank = 0, Pin name =
IO_L34N_GCLK18,          Sch name = BTND
#NET "aug"               LOC = "D9" | IOSTANDARD = "LVCMOS33"; #Bank = 0, Pin name =
IO_L34P_GCLK19,          Sch name = BTNR
56
58 ## 12 pin connectors
60 ##JA
#NET "JA<0>"             LOC = "T12" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L19P
,                          Sch name = JA1
62 #NET "noteb<0>"        LOC = "V12" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
IO_L19N,                 Sch name = JA2
#NET "JA<2>"             LOC = "N10" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L20P
,                          Sch name = JA3
64 #NET "noteb<1>"        LOC = "P11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name =
IO_L20N,                 Sch name = JA4
#NET "JA<4>"             LOC = "M10" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L22P
,                          Sch name = JA7
66 #NET "JA<5>"           LOC = "N9" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L22N
,                          Sch name = JA8
#NET "JA<6>"             LOC = "U11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L23P
,                          Sch name = JA9
68 #NET "JA<7>"           LOC = "V11" | IOSTANDARD = "LVCMOS33"; #Bank = 2, Pin name = IO_L23N
,                          Sch name = JA10
70 ##JB
NET "noteb<2>"           LOC = "K2" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L38P_M3DQ2,           Sch name = JB1
72 #NET "noteb<3>"        LOC = "K1" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L38N_M3DQ3,           Sch name = JB2
NET "noteb<4>"           LOC = "L4" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L39P_M3LDQS,          Sch name = JB3
74 #NET "noteb<5>"        LOC = "L3" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L39N_M3LDQSN,         Sch name = JB4
#NET "RsRx_p"            LOC = "J3" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L40P_M3DQ6,           Sch name = JB7
76 #NET "JB<5>"           LOC = "J1" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L40N_M3DQ7,           Sch name = JB8
#NET "JB<6>"             LOC = "K3" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L42N_GCLK24_M3LDM,    Sch name = JB9
78 #NET "JB<7>"           LOC = "K5" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L43N_GCLK22_IRDY2_M3CASN, Sch name = JB10

```

```

80 ##JC
NET "noteb<6>" LOC = "H3" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L44N_GCLK20_M3A6, Sch name = JC1
82 NET "noteb<7>" LOC = "L7" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L45P_M3A3, Sch name = JC2
#NET "JC<2>" LOC = "K6" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L45N_M3ODT, Sch name = JC3
84 NET "noteb<8>" LOC = "G3" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L46P_M3CLK, Sch name = JC4
#NET "rx_done_tick_p" LOC = "G1" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
= IO_L46N_M3CLKN, Sch name = JC7
86 #NET "JC<5>" LOC = "J7" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L47P_M3A0, Sch name = JC8
#NET "JC<6>" LOC = "J6" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L47N_M3A1, Sch name = JC9
88 #NET "JC<7>" LOC = "F2" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L48P_M3BA0, Sch name = JC10

90 ##JD, LX16 Die only
NET "noteb<9>" LOC = "G11" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L40P, Sch name = JD1
92 NET "noteb<10>" LOC = "F10" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L40N, Sch name = JD2
NET "noteb<11>" LOC = "F11" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L42P, Sch name = JD3
94 NET "noteb<12>" LOC = "E11" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name =
IO_L42N, Sch name = JD4
NET "sync" LOC = "D12" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name = IO_L47P,
Sch name = JD7
96 NET "DinA" LOC = "C12" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name = IO_L47N,
Sch name = JD8
#NET "JD<6>" LOC = "F12" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name = IO_L51P
, Sch name = JD9
98 NET "sclk" LOC = "E12" | IOSTANDARD = "LVCMOS33"; #Bank = 3, Pin name = IO_L51N,
Sch name = JD10
100

```

Keyboard Testbench:

```
-----
2  -- Company: ENGS31 15X
  -- Engineer: Stylianos Tegas and Liane Makatura
4  --
  -- Create Date:    19:35:14 08/20/2015
6  -- Design Name:
  -- Module Name:    O:/engs31/Keyboard/KeyboardTest.vhd
8  -- Project Name:  Keyboard
  -- Target Device:
10 -- Tool versions:
  -- Description:
12 --
  -- VHDL Test Bench Created by ISE for module: KeyboardTop
14 --
  -- Dependencies:
16 --
  -- Revision:
18 -- Revision 0.01 - File Created
  -- Additional Comments:
20 --
  -- Notes:
22 -- This testbench has been automatically generated using types std_logic and
  -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
24 -- that these types always be used for the top-level I/O of a design in order
  -- to guarantee that the testbench will bind correctly to the post-implementation
26 -- simulation model.
  -----
28 LIBRARY ieee;
  USE ieee.std_logic_1164.ALL;
30
  -- Uncomment the following library declaration if using
32 -- arithmetic functions with Signed or Unsigned values
  --USE ieee.numeric_std.ALL;
34
  ENTITY KeyboardTest IS
36 END KeyboardTest;
38
  ARCHITECTURE behavior OF KeyboardTest IS
40
    -- Component Declaration for the Unit Under Test (UUT)
42
    COMPONENT KeyboardTop
      PORT (
44         clk : IN  std_logic;
          noteb : in STD_LOGIC_VECTOR (12 downto 0);
46         sus : in std_logic;
          sync : OUT std_logic;
48         sclk : OUT std_logic;
          DinA : OUT std_logic
50       );
    END COMPONENT;
52
54 --Inputs
    signal clk : std_logic := '0';
56    signal noteb : std_logic_vector (12 downto 0) := (others => '0');
    signal sus : std_logic := '0';
58
  --Outputs
60    signal sync : std_logic;
    signal sclk : std_logic;
62    signal DinA : std_logic;
```

```

64  -- Clock period definitions
65  constant clk_period : time := 10 ns;
66  constant sclk_period : time := 10 ns;
67
68 BEGIN
69
70  -- Instantiate the Unit Under Test (UUT)
71  uut: KeyboardTop PORT MAP (
72      clk => clk,
73      noteb => noteb,
74      sus => sus,
75      sync => sync,
76      sclk => sclk,
77      DinA => DinA
78  );
79
80  -- Clock process definitions
81  clk_process :process
82  begin
83      clk <= '0';
84      wait for clk_period/2;
85      clk <= '1';
86      wait for clk_period/2;
87  end process;
88
89
90  -- Stimulus process
91  stim_proc: process
92  begin
93      -- hold reset state for 100 ns.
94      wait for 100 ns;
95
96      wait for clk_period*10;
97
98      -- insert stimulus here
99
100     noteb(0) <= '1';
101     wait for 2E4*clk_period;
102     noteb(0) <= '0';
103     wait for 1E4*clk_period;
104
105     noteb(0) <= '1';
106     noteb(4) <= '1';
107     noteb(7) <= '1';
108     noteb(12) <= '1';
109     wait for 3E4*clk_period;
110
111     sus <= '1';
112     wait for 1E4*clk_period;
113
114
115     noteb(0) <= '0';
116     noteb(4) <= '0';
117     noteb(7) <= '0';
118     noteb(12) <= '0';
119     wait for 2E4*clk_period;
120
121     sus <= '0';
122
123     wait;
124
125 end process;
126
127
128

```


130 | **END;**

3. Resource Utilization

According to the Design Summary, our keyboard design had the following resource usage on the FPGA (the following is taken directly from the synthesis report):

Slice Logic Utilization: Number of Slice Registers: 348 out of 18224 1%
Number of Slice LUTs: 487 out of 9112 5%
Number used as Logic: 461 out of 9112 5%
Number used as Memory: 26 out of 2176 1%
Number used as SRL: 26

Slice Logic Distribution:
Number of LUT Flip Flop pairs used: 540
Number with an unused Flip Flop: 192 out of 540 35%
Number with an unused LUT: 53 out of 540 9%
Number of fully used LUT-FF pairs: 295 out of 540 54%
Number of unique control sets: 20

IO Utilization:
Number of IOs: 18
Number of bonded IOBs: 18 out of 232 7%
Specific Feature Utilization:
Number of Block RAM/FIFO: 11 out of 32 34%
Number using Block RAM only: 11
Number of BUFG/BUFGCTRLs: 3 out of 16 18%
Number of DSP48A1s: 2 out of 32 6%

4. Critical Timing Path

According to the Synthesis Report, the critical path in our keyboard is the delay from the controller to the normalizer with the number of notes signal. The critical timing path is 7.431ns, of which 4.372ns is from the logic and 3.059ns is from the routing of the signal. Below is the full report from the synthesis report:

```
=====
Timing constraint: Default period analysis for Clock Inst.ClockDivider/tog
Clock period: 7.431ns (frequency: 134.576MHz)
Total number of paths / destination ports: 3484 / 394
-----
Delay: 7.431ns (Levels of Logic = 4)
Source: num_notes_2 (FF)
Destination: Inst_Normalizer/iQ_0 (FF)
Source Clock: Inst.ClockDivider/tog rising
Destination Clock: Inst.ClockDivider/tog rising
Data Path: num_notes_2 to Inst_Normalizer/iQ_0
Gate Net
Cell:in-;out fanout Delay Delay Logical Name (Net Name)
----- FDR:C-;Q 26 0.525 1.696 num_notes_2 (num_notes_2)
begin scope: 'Inst_Normalizer:num_note;2;'
LUT4:I0-;O 1 0.254 0.681 GND_13_o_X_13_o_wide_mux_3_OUT;2;11 (GND_13_o_X_13_o_wide_mux_3_OUT;2;)
DSP48A1:A2-;M27 1 3.265 0.682
Mmult_note_to_norm[15]_GND_13_o_MuLt_4_OUT
```

(note_to_norm[15]_GND_13_o_MuLt_4_OUT;27;)
LUT5:I4-¿O 1 0.254 0.000 Mmux_multi_note121 (multi_note;27;)
FDE:D 0.074 iQ_11

Total 7.431ns (4.372ns logic, 3.059ns route)
(58.8% logic, 41.2% route)

This implies that the maximum possible frequency at which our design can be clocked is $\frac{1}{7.431} = 0.1346$ gigahertz, or $f_{max} = 134.6 MHz$.

5. Analysis of Residual Warnings

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_10_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process. WARNING:Xst:1293 - FF/Latch <note_addresses_10_1>has a constant value of 0 in block <KeyboardTop>. This FF/Latch will be trimmed during the optimization process.

Analysis: These warnings come about because the step size for D (stored in the 10th element of the note_addresses array) is 436, which is divisible by 4. Thus, neither of the two least significant bits will ever change. Since the value will always be 0, VHDL was able to optimize the design by chopping off these extra flip flops and hard wiring in the appropriate 0 values for the last two bits.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_11_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process. WARNING:Xst:1293 - FF/Latch <note_addresses_11_1>has a constant value of 0 in block <KeyboardTop>. This FF/Latch will be trimmed during the optimization process.

Analysis: These warnings come about because the step size for C^\sharp/D^b (stored in the 11th element of the note_addresses array) is 412, which is divisible by 4. Thus, neither of the two least significant bits will ever change. Since the value will always be 0, VHDL was able to optimize the design by chopping off these extra flip flops and hard wiring in the appropriate 0 values for the last two bits.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_6_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process.

Analysis: This warning comes about because the step size for F^\sharp/G^b (stored in the 6th element of the note_addresses array) is 550, which is divisible by 2. Thus the least significant bit will never change. Since the value will always be 0, VHDL was able to optimize the design by chopping off this flip flop and hard wiring a 0.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_9_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process.

Analysis: This warning comes about because the step size for D^\sharp/E^b (stored in the 9th element of the note_addresses array) is 462, which is divisible by 2. Thus the least significant bit will never change. Since the value will always be 0, VHDL was able to optimize the design by chopping off this flip flop and hard wiring a 0.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_8_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process.

Analysis: This warning comes about because the step size for E (stored in the 6th element of the note_addresses array) is 490, which is divisible by 2. Thus the least significant bit will never change. Since the value will always be 0, VHDL was able to optimize the design by chopping off this flip flop and hard wiring a 0.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_1_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process.

Analysis: This warning comes about because the step size for B (stored in the 1st element of the note_addresses array) is 734, which is divisible by 2. Thus the least significant bit will never change. Since the value will always be 0, VHDL was able to optimize the design by chopping off this flip flop and hard wiring a 0.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_3_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process.

Analysis: This warning comes about because the step size for A (stored in the 0th element of the note_addresses array) is 654, which is divisible by 2. Thus the least significant bit will never change. Since the value will always be 0, VHDL was able to optimize the design by chopping off this flip flop and hard wiring a 0.

Excerpt:

WARNING:Xst:1293 - FF/Latch <note_addresses_0_0>has a constant value of 0 in block <Keyboard-Top>. This FF/Latch will be trimmed during the optimization process.

Analysis: This warning comes about because the step size for C^5 (stored in the 0th element of the note_addresses array) is 778, which is divisible by 2. Thus the least significant bit will never change. Since the value will always be 0, VHDL was able to optimize the design by chopping off this flip flop and hard wiring a 0.

7.3 Memory Map

Our project used a sine Lookup Table (LUT) that was generated by the DDS Compiler 4.0, found in the IP Core Generator. This LUT contains 2^{16} incremental values of a sin wave, where each value is 12 bits long. This requires a substantial amount of block memory (on the order of $64,000 * 12$ bits), but surprisingly we only ended up using 11 block rams to do it. While we are not exactly sure how the Core Generator and Xilinx optimized our memory, we do believe that it was able to recognize and exploit the symmetry of the sin wave values, thus only needing to store $\frac{1}{4}$ of the original memory amount. In addition to the apparent flip flops and registers that are pictured in our block diagram, we also utilized block memory to store our arrays for the note steps and the current note addresses. The note step values are what we used to update the value of the note address each time we wanted to sample, so that we could get the appropriate frequencies for each note. These values remained constant. The note addresses array stored the current address for each of the 13 notes, and this value

was updated then passed into the sin LUT to get the appropriate value for the note on each sampling cycle.

7.4 Waveform Graphs

 


Figure 6: These images (chronologically arranged from top to bottom) show the output of our testbench for the KeyboardTop module, which runs the entire project with all components included. This testbench is included in the VHDL code section, and the waveform shows all values of the inputs and outputs of the system, beginning with the buttons and ending with the outputs of the DAC.

7.5 Data Sheets

All of our external components were manufactured by Digilent, so there were no additional data sheets to include.

7.6 Computer Programs

```

1  % Liane Makatura
2  % Finding the m values for various frequencies
3
4  freqs = [261.63 277.18 293.66 311.13 329.63 349.23 369.99 392.00 415.30 440.00 466.16
5  493.88 523.25];
6
7  samp_rate = 44100;
8  n_bits = 16;
9
10 mvals = freqs .* (2^n_bits) ./ samp_rate;
11
12 disp(mvals)

```

| Note | Resulting Step | Integer M Value |
|----------------|----------------|-----------------|
| C4 | 388.8024 | 389 |
| C^\sharp/D^b | 411.9108 | 412 |
| D | 436.4014 | 436 |
| D^\sharp/E^b | 462.3632 | 462 |
| E | 489.8556 | 490 |
| F | 518.9827 | 519 |
| F^\sharp/G^b | 549.8337 | 550 |
| G | 582.5422 | 583 |
| G^\sharp/A^b | 617.1678 | 617 |
| A | 653.8739 | 654 |
| A^\sharp/B^b | 692.7497 | 693 |
| B | 733.9438 | 734 |
| C5 | 777.5898 | 778 |

Table 2: M-values for our 13 notes, obtained from the MATLAB code sample above. These calculations are based on a 44.1kHz sampling rate, and 2^{16} samples of the sine wave.

```

1  % Liane Makatura
2  % Calculate strength reduction factors
3
4  denom = 4096;
5
6  for num=2:13
7      ideal_mult = 1/sqrt(num);
8      number = floor(ideal_mult*4000);
9      error = abs((number / denom) - ideal_mult);
10     nextdiff = abs(((number+1) / denom) - ideal_mult);
11     while error > 0.001 || error > nextdiff
12         number = number + 1;
13         error = nextdiff;

```

```

15         nextdiff = abs(((numer+1) / denom) - ideal_mult);
16     end
17
18     fprintf('Notes: %d\n', num)
19     fprintf('Ideal Divisor: %6.5f\n', ideal_mult)
20     fprintf('Multiplier: %d\n', numer)
21     fprintf('Appx Divisor: %6.5f\n', (numer/denom))
22     fprintf('Error: %6.5f\n\n', abs((numer/denom)-ideal_mult))
23 end

```

From this simple MATLAB program, we were able to generate the following approximations, which we used to normalize the accumulated frequencies for polyphony:

| Number of Notes | Ideal Multiplier | Integer Multiplier | Approximated Multiplier | Error |
|-----------------|---------------------------------------|--------------------|-------------------------|---------|
| 1 | $\frac{1}{\sqrt{1}} = 1.00000$ | 4096 | 1.00000 | 0.00000 |
| 2 | $\frac{1}{\sqrt{2}} \approx 0.70711$ | 2896 | 0.70703 | 0.00008 |
| 3 | $\frac{1}{\sqrt{3}} \approx 0.57735$ | 2365 | 0.57739 | 0.00004 |
| 4 | $\frac{1}{\sqrt{4}} = 0.50000$ | 2048 | 0.50000 | 0.00000 |
| 5 | $\frac{1}{\sqrt{5}} \approx 0.44721$ | 1832 | 0.44727 | 0.00005 |
| 6 | $\frac{1}{\sqrt{6}} \approx 0.40825$ | 1672 | 0.40820 | 0.00005 |
| 7 | $\frac{1}{\sqrt{7}} \approx 0.37796$ | 1548 | 0.37793 | 0.00003 |
| 8 | $\frac{1}{\sqrt{8}} \approx 0.35355$ | 1448 | 0.35352 | 0.00004 |
| 9 | $\frac{1}{\sqrt{9}} = 0.33333$ | 1365 | 0.33325 | 0.00008 |
| 10 | $\frac{1}{\sqrt{10}} \approx 0.31623$ | 1295 | 0.31616 | 0.00007 |
| 11 | $\frac{1}{\sqrt{11}} \approx 0.30151$ | 1235 | 0.30151 | 0.00000 |
| 12 | $\frac{1}{\sqrt{12}} \approx 0.28868$ | 1182 | 0.28857 | 0.00010 |
| 13 | $\frac{1}{\sqrt{13}} \approx 0.27735$ | 1136 | 0.27734 | 0.00001 |

Table 3: Consolidated results from the code snippet above. All approximations assume a 12-bit shift (or division by 4096) after the integer multiplication.